
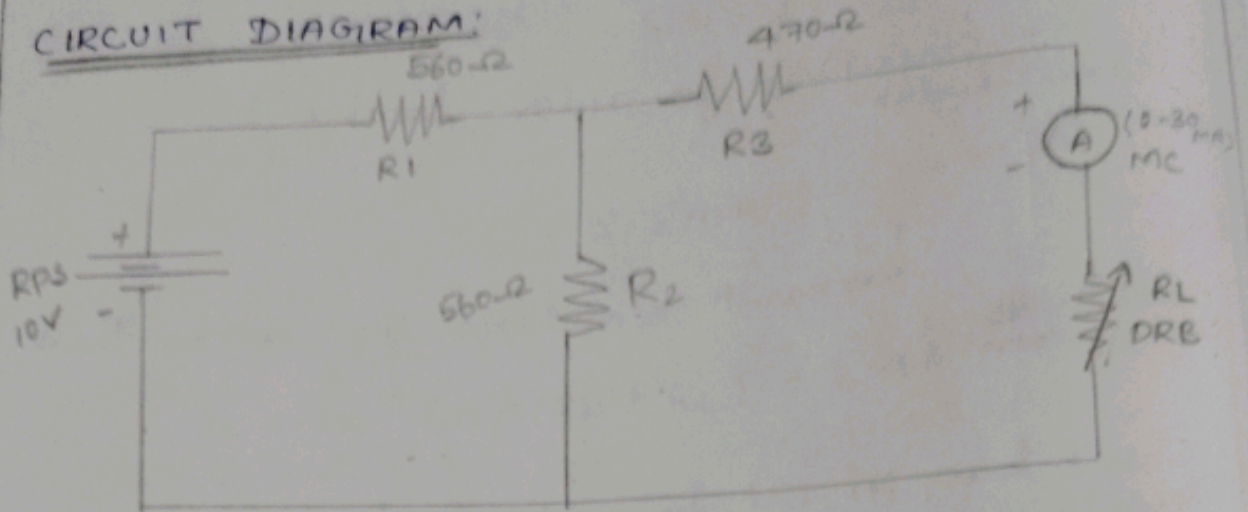


### CIRCUIT DIAGRAM:

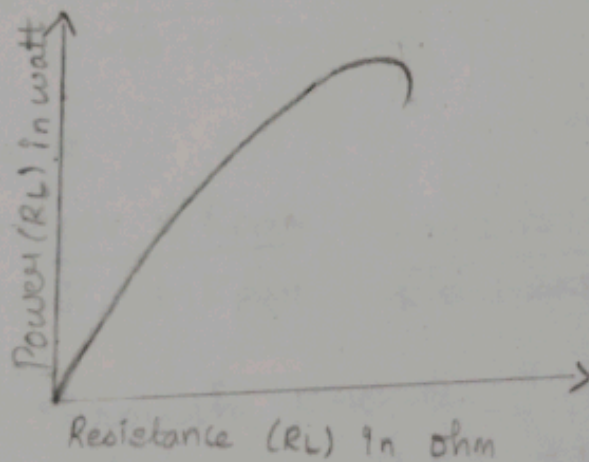

### MODEL GRAPH:





EXP NO: 6

DATE:  
26-09-25VERIFICATION OF MAXIMUM POWER  
TRANSFER THEOREMAIM:

To measure the power absorbed in a load and the verify that the power absorbed in a load is maximum only when load resistance is equal to the source resistance.

APPARATUS REQUIRED:

S. NO	NAME OF THE APPARATUS	RANGE / RATING	QUANTITY
1.	Voltmeter	(0-15V) MC	1
2.	Ammeter	(0-500 mA) MC	1
3.	Resistor	560 $\Omega$ , 470 $\Omega$	2, 1
4.	RPS (DC supply)	15V	1

PROCEDURE:

1) Make connection as per the circuit diagram.

2) Change the resistors  $R_L$  whose value close to  $R_{th}$ , measure the corresponding  $V_L$ ,  $I_L$  and calculate the power  $P_L$  and enter into the table (2).



TABLE (2): FOR PRACTICAL CALCULATION

S. No	load resistance (RL) in ohm	load current (IL) in amps	load voltage (VL) in volts	load Power (PL) in watts
1.	1 K-Ω	2.96 mA	2.96 V	8.76 mW
2.	150 K-Ω	553 mA	0.995 V	5.504 mW
3.	100 K-Ω	6.00 mA	0.6 V	3.6 mW
4.	470 K-Ω	4.13 mA	1.944	8.01 mW
5.	51-Ω	0.85 mA	4.335 V	3.684 mW

CALCULATION:

$$V_{th} = \frac{V \times R_2}{R_1 + R_2} = \frac{10 \times 500}{2(560)} = 5V$$

$$R_{th} = \frac{560 \times 560}{2(560)} + 470 = 280 + 470 = 750-\Omega$$

$$R_L = R_{th}$$

$$P_L = \frac{(V_{th})^2}{4(R_{th})} = \frac{(5)^2}{4 \times 750} = \frac{25}{3000} = 0.0083 = 8.33 mW$$

$$I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{5}{1500} = 0.00333 A$$

$$I_L = 3.33 mA$$

$$V_L = I_L \times R_L = 3.33 \times 10^{-3} \times 750$$

$$V_L = 2.5 V$$



3. Plot a graph between  $R_L$  and  $P_L$  and find the  $R_L$  corresponding to maximum power transfer.
4. Verify the measured values of  $R_L$  at maximum power transfer as same as calculated and found graphically.

### RESULT:

Thus Maximum power transfer theorem is verified practically and theoretically.